 


RTL digital system design

- Generic systems do control tasks and data processing
 - Processing unit or *datapath*
 - Perform the operations among data data
 - Data enters the system and is stored in registers or memories
 - Functional units implement the operations (coded as Verilog *expressions*)
 - Control unit or *control path*
 - Schedule the operations through the datapath
 - Selects the data to feed the functional units, select operations
 - Determine which registers or memories are loaded in each clock
- *Control dominated systems*
 - Most of the system function is control (e.g. traffic light controller)
- *Data flow dominated*
 - Most of the system is datapath, little or no control (FIR filter)

Register-transfer level



Control unit

Datapath



Elements of the datapath

- Registers and memories
 - Hold data, write is synchronous with a clock signal
- Buses, multiplexers, 3-state buffers
 - Interconnect components and steer data along the datapath
- Functional units (FU)
 - Basic model
 - Direct translation of a Verilog expression, fully combinational
 - `assign y1 = (a + b * { y[31:16], z[15:0] } >>> 6);`
 - More complex models for FUs (need to be built “by hand”!)
 - Perform the operation in more than a single clock cycle (sequential)
 - Perform operations in *pipeline*
 - Support for different operations sharing logic structures (add and mul)
 - Using dynamic reconfiguration (in FPGAs)


Clocked synchronous systems

- A clock signal triggers all the registers
 - The control path defines the next state of the registers
 - Which registers are loaded and with which data
 - The datapath performs the operations on the data
 - The registers/memories are loaded in the active clock edge
 - Digital circuits need time to propagate logic signals
 - Due to parasitic Rs and Cs and transistor dynamic behaviour

  Uncertainty (data not yet stable, possible glitching)




Flip-flop timing

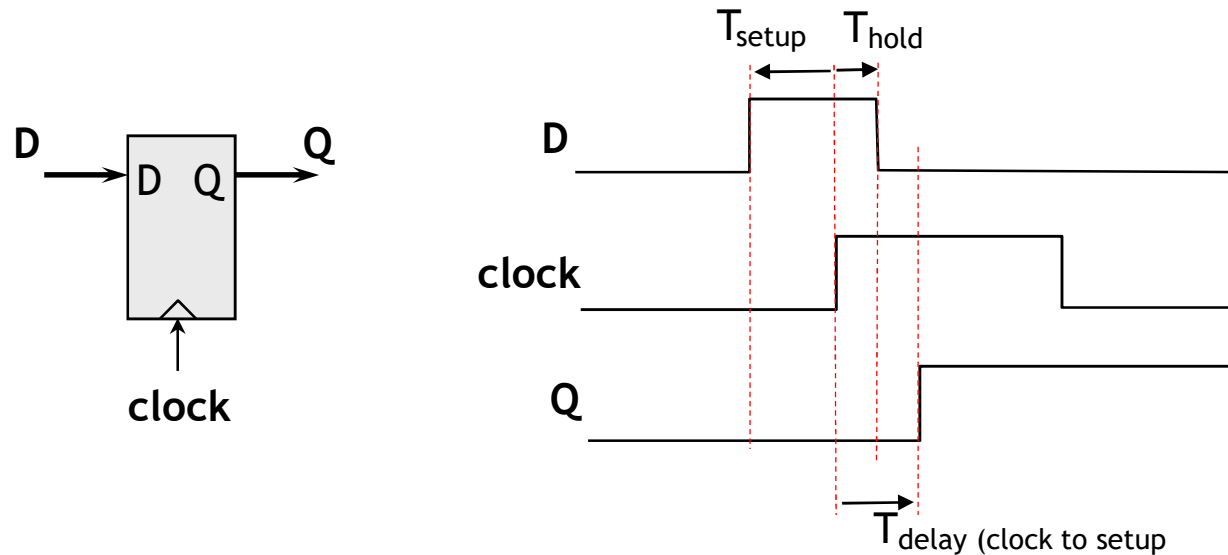


- Flip-flop timing constraints & characteristics
 - D input must be stable before the clock by T_{setup}
 - D input must remain stable for T_{hold} after the clock
 - The clock signal must have a minimum rise/fall time
 - Q output changes T_{delay} after the clock edge (not a constraint)
- What happens if these timing constraints are violated?

 Clocked synchronous systems (combinational logic between registers)



- The circuit delay determines the maximum clock frequency
 
$$\text{Maximum clock frequency} < 1 / \max(T_{\text{delay1}}, T_{\text{delay2}}, T_{\text{delay3}})$$




Clocked synchronous systems

- Simple to design, but...
 - All registers have the same clock [logic] signal
 - the clock must be in phase in all flop-flops (nor necessarily...)
 - It is necessary to guarantee T_{setup} and T_{hold} of all flip-flops
 - high fanout net: requires a dedicated network to distribute the clock
 - The clock is a free-running signal continuously switching
 - High power consumption (a significant part of power is due to the transitions)
 - “Clock gating” can switch off the clock but needs careful design
 - The real propagation delays are only known after place & route
 - Handling asynchronous inputs
 - Preventing metastability
 - Synchronizing data transfers among multiple clock domains
 - Need to guarantee correct data transport between different clock domains
 - Need for dedicated blocks to handle the clock domain crossing (*CDC*)


Clock skew

 - Variation of the clock phase in different registers




Clock skew

 
- Un-balanced clock distribution network
 - Different physical characteristics (length, R, C, L)



- Different fanout

 

 - Logic in the clock path (for now this is illegal!)




Gated clock

- Conditional register loading
 - Wrong solution: insert and AND in the clock path


```
assign clock_ce = clock & ce;  
always @(posedge clock_ce)  
...
```

ce

 

R1 may be loaded twice
Depends on the propagation delays





- *synchronous clock enable*

 

- *flip-flops with native clock enable*


```
always @(posedge clock)  
if ( ce )  
...
```

Safe gated clocking

   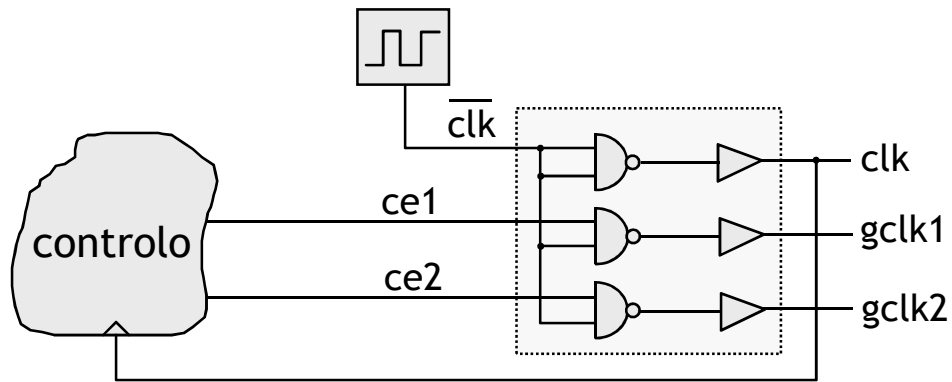


Asynchronous inputs

 - What happens if the FF timing is violated?
 - FFs can stay for some time in a metastable state (not representing 1 or 0)
 - FFs are bistable, if left in an unstable state they will fall to 1 or 0
- How to synchronize asynchronous inputs
 - Basic solution: use a two-stage shift-register to sync external inputs




Explain how this works!

Multiple clock domains

 

- GALS – *Globally Asynchronous Locally Synchronous*
 - Different clock signals from independent sources (for example, different oscillators)
- Problems
 - How to generate and distribute the different clock signals ?
 - How to implement a correct clock domain crossing (or CDC) ?

Multiple operation rate

 

- Use a single clock for all the flip-flops
 - The whole circuit is synchronous with the (single) main clock
 - The clock frequency must be the minimum common multiple of all rates
- Use clock enables derived from the main clock
 - A clock enable pulse must last only for one main clock period
 - Easily generated with counters and comparators

Pipelining

