 






# Principles of low power digital design

- Why low power?
  - Decrease cost of packaging, power supply, cooling system,...
  - Increase autonomy and portability
  - Save energy
  - Limit the maximum power demand (or current) from the power supplies
  - Increase reliability: MTBF (*Mean Time Between Failure*) decreases with T


   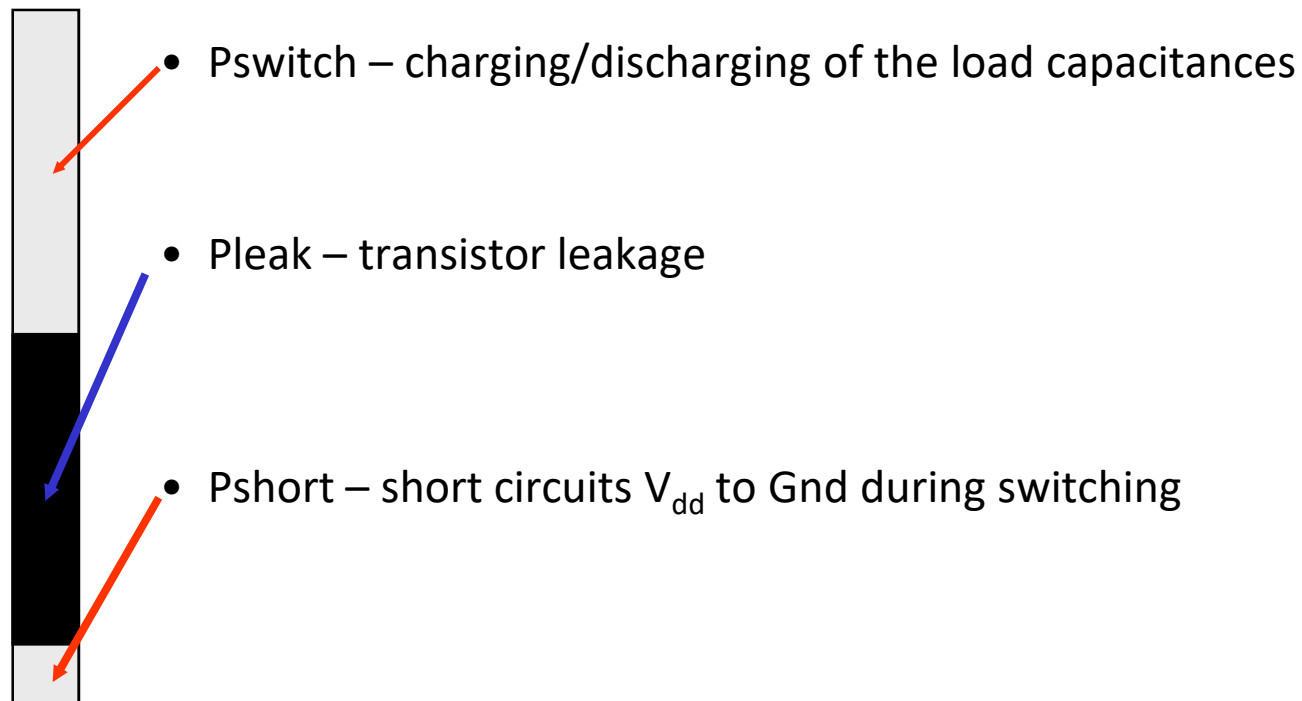
# Sources of energy consumption

- CMOS digital technology
  - Average electric power:  $P_{\text{total}} = P_{\text{switch}} + P_{\text{leak}} + P_{\text{short}}$





# How to reduce the power consumption?

## – Pleak (or static power)


- Subthreshold leakage, gate to substrate reverse-bias leakage
- Depends on the physical characteristics of technology
  - Reducing the technology node from 28nm (planar) to 12 nm (finFET): -50% of leakage
- Pleak is roughly proportional to the *size* of the circuit
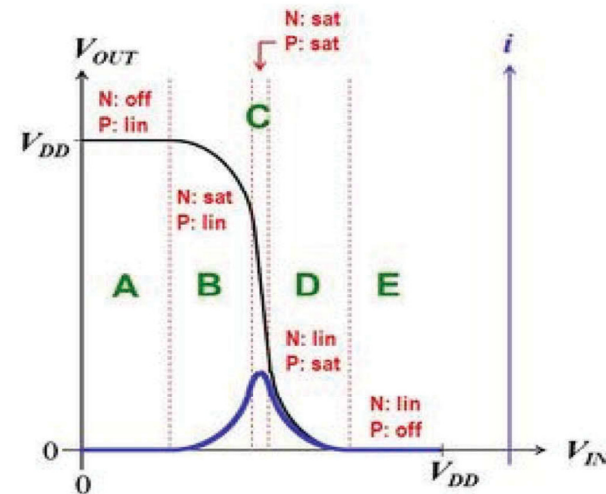 
## – Pshort

- Due to the limited transition time between ON an OFF states
- Pshort depends on the switching activity and rise/fall times of inputs





# Leakage and active power

 
  
# Low power design

– Dynamic power consumption – depends on the circuit activity

- $P_{\text{switch}} = \alpha \cdot C_L \cdot V_{\text{dd}}^2 \cdot f_{\text{clk}}$ 
  - $C_L$  = load capacitance
  - $V_{\text{dd}}$  = power supply
  - $\alpha$  = average transitions per clock cycle
  - $f_{\text{clk}}$  = clock frequency
- $\alpha \cdot C_L = C_{\text{effective}}$  effective load capacitance



# How to reduce Pswitch?

$$P_{\text{switch}} = \alpha \cdot C_L \cdot V_{\text{dd}}^2 \cdot f_{\text{clk}}$$

- Vdd: power depends on  $V_{\text{dd}}^2$ 
  - 5V to 3.3V: 43%  $P_{\text{switch}}_{5\text{V}}$
  - 3.3V to 1.8V: 31%  $P_{\text{switch}}_{3.3\text{V}}$
  - 5V to 1.2V: 6%  $P_{\text{switch}}_{5\text{V}}$
- Switching activity:  $\alpha$  and/or  $f_{\text{clk}}$ 
  - Use clock frequency as low as possible (gated clocking is mandatory!)
  - Isolate glitching propagation through combinational circuits
  - Exploit low switching topologies and appropriate data encoding
- $C_L$ : Load capacitance  $C_L$

# Switching activity and logic function

- NOR gate with random inputs
  - $P(0 \rightarrow 1) = P(1 \rightarrow 0) = p(1) \cdot p(0) = 1/4 \cdot 3/4 = 3/16 = \mathbf{0.19}$
  - $P(0 \rightarrow 0) = 3/4 \cdot 3/4 = 9/16$
  - $P(1 \rightarrow 1) = 1/4 \cdot 1/4 = 1/16$
- XOR gate with random inputs
  - $P(1 \rightarrow 0) = P(0 \rightarrow 1) = 1/2 \cdot 1/2 = 1/4 = 0.25$
  - $P(0 \rightarrow 0) = P(1 \rightarrow 1) = 1/2 \cdot 1/2 = 1/4 = 0.25$
- A complex logic function can be realized with different circuits
  - The transition probabilities of the internal nodes may vary
- In general the inputs have different probability of switching

# Switching activity and logic function



- NOR gate with random inputs
  - $P(0 \rightarrow 1) = P(1 \rightarrow 0) = p(1) * p(0) = 1/4 * 3/4 = 3/16 = 0.19$
  - $P(0 \rightarrow 0) = 3/4 * 3/4 = 9/16$
  - $P(1 \rightarrow 1) = 1/4 * 1/4 = 1/16$
- XOR gate with random inputs
  - $P(1 \rightarrow 0) = P(0 \rightarrow 1) = 1/2 * 1/2 = 1/4 = 0.25$
  - $P(0 \rightarrow 0) = P(1 \rightarrow 1) = 1/2 * 1/2 = 1/4 = 0.25$
- A complex logic function can be realized with different circuit topologies
  - Transition probabilities of the internal nodes may vary
- In general the inputs have different switching probabilities
  - Compare two's complement to sign and magnitude in a digital signal

Output of a XOR gate has higher activity



# Static switching analysis



## two topologies for the same function

  

	O1	O2
P(0->1) cascaded	3/16=0.19	7/64=0.11
P(0->1) tree	3/16=0.19	3/16=0.19
  
# Dynamic switching analysis


- Delays induce glitching in the outputs (unwanted transitions)
- Glitches propagate through the circuits
- 4-input AND implemented as  $((A.B).C).D$ 
  - The transition **1110**→**1011** generates a glitch
- 4-input AND implemented as  $(A.B).(C.D)$ 
  - If the AND gates are balanced, **1110**→**1011** is glitch free


 
# Reducing Vdd

- Pswitch depends on  $V_{dd}^2$

– But the propagation delay decreases with  $V_{dd}$  : 
$$T_d = \frac{C_L V_{dd}}{K(W/L)(V_{dd} - V_{th})^2}$$




Improve the system architecture using  
pipelining or parallel processing

Some CMOS technologies provide dual voltage cells

Power gating: switch off Vdd or to a low voltage  
Level, high enough to keep the state of FFs

# Architectural optimizations

- Reference circuit

 

Supply voltage:  $V_{dd_{ref}}=5V$

Maximum propagation delay: 25ns (adder and comparator)

Minimum clock period: 25ns ( $f_{ref}=1/25ns = 40 \text{ MHz}$ )

Total effective capacitance:  $C_{ref}$


Switching power:  $P_{ref} = \frac{1}{2} C_{ref} \cdot V_{dd_{ref}}^2 \cdot f_{ref}$

**If the circuit operates at 40 MHz Vdd cannot be reduced as this would increase the delay**

---

Based on Chandrakasan, A. P., Sheng, S., & Brodersen, R. W. (1992). Low-power CMOS digital design. IEICE Transactions on Electronics, 75(4), 371-382.

# Parallel circuit (DDR operation)

 


The same throughput with a propagation delay of 50ns ( $F_{\text{clock}} = 20 \text{ MHz}$ )

To increase the propagation delay  $V_{\text{dd}}$  can be reduced to  $V_{\text{dd}_{\text{par}}} = 0.58 V_{\text{dd}_{\text{ref}}} (2.9\text{V})$

$C_{\text{par}} = 2.15C_{\text{ref}}$  (above 2X due to the increased logic)

$P_{\text{par}} = \frac{1}{2} \cdot (2.15C_{\text{ref}}) \cdot (0.58V_{\text{dd}_{\text{ref}}})^2 f_{\text{ref}}/2 \approx 0.36P_{\text{ref}}$

# Pipelined circuit

 

With a perfectly ballanced pipeline the clock frequency can increase to 80 MHz

**Vdd can decrease to increase the propagation delay to the original Fclock**


The same throughput using the same clock frequency ( $f_{\text{pipe}} = f_{\text{ref}}$ )

$$V_{\text{dd,pipe}} = 0.58V_{\text{dd,ref}} \text{ (2.9V)}$$

$$C_{\text{pipe}} = 1.15C_{\text{ref}}$$

$$P_{\text{pipe}} = \frac{1}{2} \cdot (1.15C_{\text{ref}}) \cdot (0.58V_{\text{dd,ref}})^2 f_{\text{ref}} \approx 0.39P_{\text{ref}}$$

# Combining parallel and pipelined

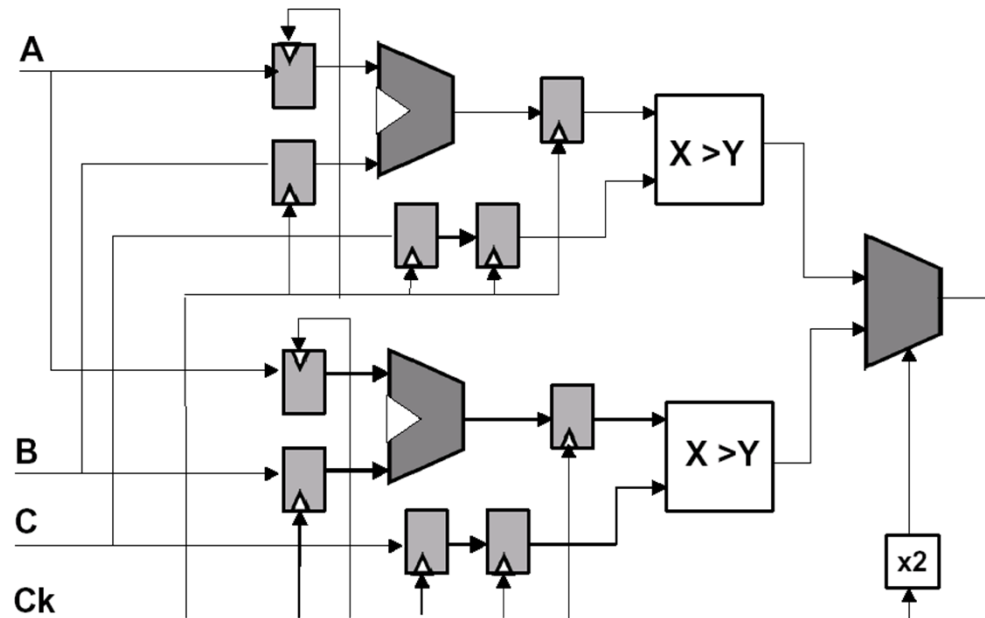

The adder and comparator may have now only  $\frac{1}{4}$  of the original propagation delay

$$f_{pp} = f_{ref} / 2$$

$$V_{dd_{pipepar}} = 0.4V_{dd_{ref}} (2.0V)$$

$$C_{pipepar} = 2.5C_{ref}$$

$$P_{pipepar} = \frac{1}{2} \cdot (2.5C_{ref}) \cdot (0.4V_{dd_{ref}})^2 f_{ref} / 2 \approx 0.2P_{ref}$$


# Summary

Architecture	$V_{dd}$	$C_{Eff}$	Area	Power
Reference	5V	1	1	1
Parallel	2.9V	2.15	3.4	0.36
Pipelined	2.9V	1.15	1.3	0.39
Parpipe	2.0V	2.50	4.0	0.2


 
# Pre-computation


- Compute a result using only part of the operands
- Do not propagate the part of the operands not needed
- Example: magnitude comparator of unsigned numbers
  - The results can be decided for 50% of the possible inputs using only the MSBits: if  $C_{n-1}$  and  $D_{n-1}$  are diferente, R2 does not need to be reloaded, avoiding the propagation of switching activity



# Clock gating

- Switch off the clock signal when not needed
  - Registers usually do not update their state in every clock transition
  - The clock signal is continuously switching and feeding all the flip-flops
    - Power is wasted in the clock line when registers are not being updated
    - A synchronous clock enable can disable the register load but keeps the clock running
      - `always @(posedge clk) if (en) Q <= D`
  - Switching on/off the clock cannot be done with an AND gate in the clock path
    - Need to avoid glitching and guarantee the synchronous operation
  - Synthesis tools and libraries provide resources for building clock gating
- Examples
  - In FSMs, if the keep-in-state condition is true the clock may be switched off
  - Banks of configuration registers are only updated for setting up parameters
  - Sequential functional units only require the clock when performing a calculation

# Clock gating

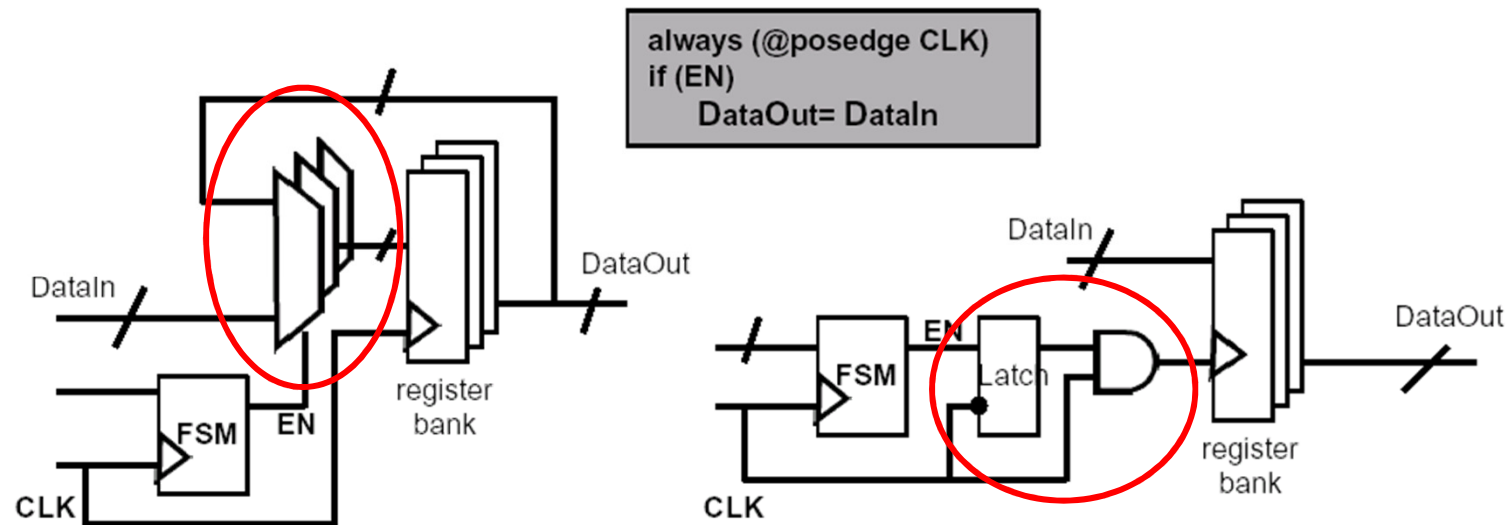


**Synchronous clock enable:**  
A 2÷1 mux is required for every FF

**Clock gating:**  
A single clock gating control creates  
a gated clock that may feed a set of FFs

Clock gating may also save silicon area
 
# Operand isolation


- transparent latches can block propagation of unnecessary data



If  $S0=0$  or  $S1 = 1$  the adder inputs A and B may be blocked  
If  $G0$  is disabled, A, B and C may be blocked.
 
# Operand isolation

- transparent latches can block propagation of unnecessary data



If  $S0=0$  or  $S1 = 1$  the adder inputs A and B may be blocked  
If G0 is disabled, A, B and C may be blocked.

# Power gating

- Switch Vdd to zero when a block is not needed
- Control Vdd for different *power islands*
  - *ON state, high performance (high Vdd)*
  - *ON state, low performance (lower Vdd)*
  - *Retention state (low Vdd, keep state of registers)*
  - *OFF state (zero Vdd, state is lost)*
- Power management unit
  - Always on, controls the power state of each power island
- Interface between ON and OFF domains
  - Isolation cells
  - Retention cells