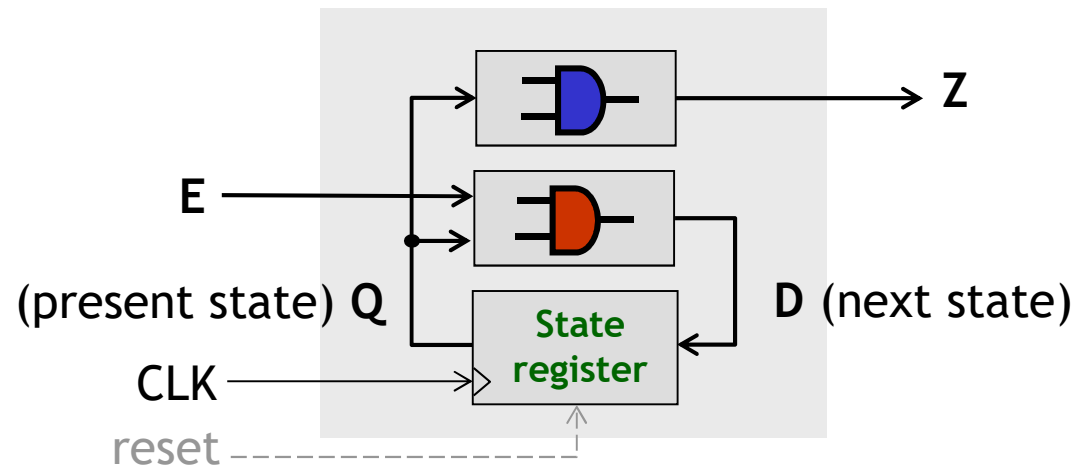


Finite state machines

(Moore model)



- **State register**
 - Loads the next state (**D** input) when the clock triggers (single register)
- **Next state combinational logic**
 - Generates the next state **D** from the present state **Q** and the inputs **E**
- **Output logic**
 - Generates the outputs **Z** from the current state **Q** (Moore model)

```

module fsm( input CLK, input RST, input E, output Z);
reg  [1:0] STATE;      // state register
reg  [1:0] NEXTSTATE; // next state (this will not be a register)


always @(posedge CLK or posedge RST)
begin
    if ( RST )
        STATE <= 2'b00;
    else
        STATE <= NEXTSTATE;
end

always @* // next state combinational logic
    case ( STATE )
        // defines NEXTSTATE using state and E
    endcase

always @* // output logic
    case( STATE)
        // defines the outputs Z with STATE
    endcase
endmodule

```

Example

 

- 3 states (INI is the initial state)
 - The minimum number of bits to encode all states is 2
- input X
- output Y depending only on the current state (Moore model)

Something is wrong here!

```
module fsm( input CLK, input RST, input X, output reg Y);
reg  [1:0] STATE;          // current state
reg  [1:0] NEXTSTATE;      // next state
parameter INI = 2'b00,    // symbolic state names
           S1  = 2'b01,    //
           S2  = 2'b11;

always @(posedge CLK or posedge RST) // state register
begin
    if ( RST )
        STATE <= INI; else STATE <= NEXTSTATE;
end


always @* // NEXTSTATE logic
case ( STATE )
    INI: if ( X == 1'b0 ) NEXTSTATE = INI; else NEXTSTATE = S1;
    S1 : if ( X ) NEXTSTATE = S1; else NEXTSTATE = S2;
    S2 : NEXTSTATE = INI;
endcase

always @* // output logic
case( STATE)
    INI: Y = 0;
    S1 : Y = 0;
    S2 : Y = 1;
endcase
endmodule
```

A different way to define the output Y

```
module fsm( . . . );  
  reg [1:0] STATE;  
  reg [1:0] NEXTSTATE;  
  parameter INI = 2'b00,  
             S1  = 2'b01,  
             S2  = 2'b11;  
  
  ...  
  
  assign Y = ( STATE == S2 ); // Y is 1 when STATE is equal to S2  
  
endmodule
```

 How to add a 'restart' input (synchronous *reset*)



```

module fsm( . . . );

. . .


always @(posedge CLK or posedge RST) // state register
begin
    if ( RST )
        STATE <= INI; else STATE <= NEXTSTATE;
end
always @* // NEXTSTATE logic
    if ( RESTART ) NEXTSTATE = INI;
    else
        case ( STATE )
            INI: if ( X == 1'b0 ) NEXTSTATE = INI; else NEXTSTATE = S1;
            S1 : if ( X ) NEXTSTATE = S1; else NEXTSTATE = S2;
            S2 : NEXTSTATE = INI;
        endcase

always @* // output logic
    ...
endmodule

```

Mealey finite state machines

Output Y also depends on E

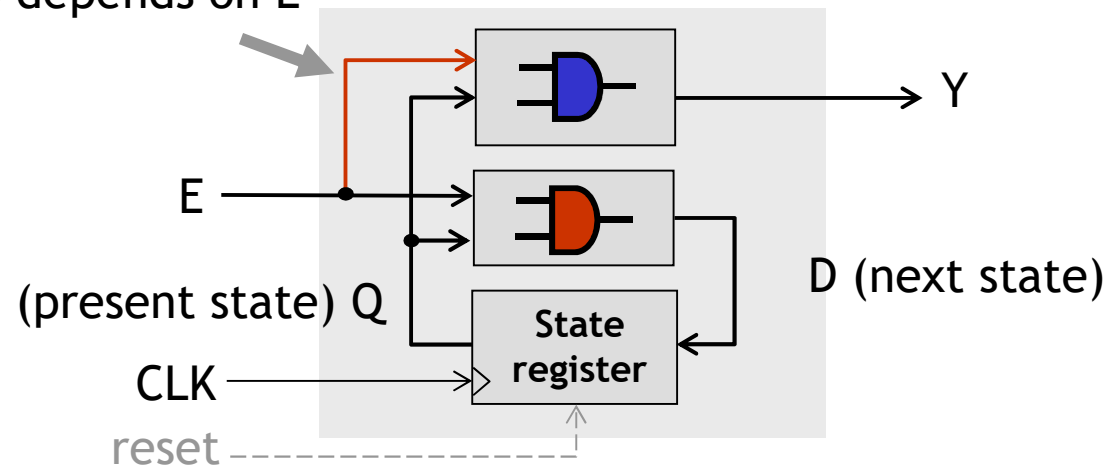


```
always @* // next state logic
case ( STATE )
  INI: if ( X ) NEXTSTATE = S1; else NEXTSTATE = INI;
  S1 : if ( X ) NEXTSTATE = S1; else NEXTSTATE = S2;
  S2 : if ( X ) NEXTSTATE = INI; else NEXTSTATE = S2;
endcase
```

```
always @* // output logic
case( STATE )
  INI: Y = 0;
  S1 : if ( X ) Y = 0; else Y = 1;
  S2 : if ( X ) Y = 1; else Y = 0;
endcase
```

```
endmodule
```

Mealy or Moore ?

```
always @(posedge clock)
if ( reset )
    state <= INI;
else
    case ( state )
        INI: if ( ~X )
                state <= INI;
            else
                state <= S1;
        S1:  if ( X )
                state <= S1;
            else
                state <= S2;
        S2:  state <= INI;
    endcase

assign Y = ( state == S2 & X );
```

```
always @(posedge clock)
if ( reset )
    begin
        state <= INI;
        Y <= 1'b0;
    end
else
    case ( state )
        INI: if ( ~X )
                begin
                    state <= INI;
                    Y <= 1'b0;
                end
            else
                begin
                    state <= S1;
                    y <= 1'b1;
                end
    endcase

    ...
endcase
```

Verilog operators (similar to C operators)

	operador	#opr	notes
arithmetic	+ - * / %	2	sign extension if signed, zero extension if unsig.
logic	!	1	logic NOT / AND / OR: zero means false, other is true returns 1 (true) or 0 (false)
	&&	2	
		2	
relational	> < >= <=	2	different behaviour for signed and unsigned
equality	== !=	2	0-1 comparison (compare with 'x' is alws. false) also compare 'z' and 'x'
	=== !==	2	
bitwise	~ & ^	1, 2	signed/unsigned extension
shift	>> <<	2	logical shift (shift right inserts zeros at the left)
arithm. shift	>>> <<<	2	arithmetic shift (shift right keeps the sign bit)
concatenation	{ }	N	{3'b101, 1'b0, 3'b111}=7'b1010111
replication	{{ }}	N	{N{A}} replicates N times the bit pattern A
conditional	<cond> ? True : False	3	as in C

Numeric constants

- Default is integer, 32 bit, twos-complement

```
reg [3:0] a;  
...  
initial  
begin  
    a = 28; // 28=11100 -> a is loaded with 1100=1210  
...  
end
```

- Defining the number of bits and numeric base (recommended):

```
5'd10;           // 5 bits, decimal  
10'b1010_0011_11; // 10 bits, binary  
16'h1E_C6;       // 16 bits, hexadecimal
```

↑ ↑ ↘ value (“_” can be used as separator for readability)
numeric base
number of bits

Signed and unsigned

- Wires and regs are handled by default as unsigned numbers
 - `wire [31:0] x, y, z; reg [14:0] r1, r2;`
 - Sign extension is not performed when increasing the number of bits
 - Comparisons of magnitude are done as unsigned numbers
- Any wire, register in or out can be declared as **signed**
 - `wire signed [31:0] a, b; reg signed [3:0] ra, rb;`
 - Arithmetic expressions should contain only signed or unsigned
 - The function `$signed(...)` converts unsigned to signed

ACCUM0:

```
begin // Accumulate the LEFT slices
    accumLL <= accumLL + gainLL * $signed( dataoutL1_L );
    accumRL <= accumRL + gainRL * $signed( dataoutR1_L );
    state <= ACCUM1;
end
```

Verilog *tasks*

- Main purpose: “encapsulate” simulation tasks
 - May contain delays and time synchronization
 - Much like a C function, without returning a value

```
task writecommand;
input [15:0] data;    // data to write
input [1:0] address; // address of output port
begin
    din = {4'b0010, 2'b00, address}; // compose and write command
    load = 1; #10 load = 0; #10 // 1d for 1 clock
    din = data[15:8]; // send MS byte
    load = 1; #10 load = 0; #20 // 1d for 2 clocks
    din = data[7:0]; // send LS byte
    load = 1; #10 load = 0; #30 load = 0;
end
endtask
```

```
initial
begin
    ...
    writecommand(16'h39A6, 2'b00 );
```

Two good references for Verilog HDL

- www.asic-world.com
- www.chipverify.com/verilog/verilog-tutorial